

EE3113 Homework Assignment-3

Krishna Srikar Durbha

EE18BTECH11014

Note: Mathematical Explanations for some of the questions are at the end.

1 1. Impact of Sizing on Performance

Specifications:

$$V_M = \frac{V_{DD}}{2} \tag{1}$$

$$V_{DD} = 1.8 \text{ Volts} \tag{2}$$

$$V_M = 0.9 \text{ Volts} \tag{3}$$

For the above condition to be satisfied, $\frac{W}{L}$ ratios should be,

$$W_n = 0.18\mu\text{m} \tag{4}$$

$$L_n = 0.18\mu\text{m} \tag{5}$$

$$W_p = 1.165\mu\text{m} \tag{6}$$

$$L_p = 0.18\mu\text{m} \tag{7}$$

1.1 1a

1.1.1 i

SPICE Netlist:

```
1 Question-1a(i)
2
3 * Model
4 .include "TSMC180.lib"
5 .model nch_tt nmos
6 .model pch_tt pmos
7
8 * Circuit
9 Vdd      S      0      DC      1.8
10 MP       D      G      S      S      pch_tt W=1.165u L=0.18u
11 MN       D      G      0      0      nch_tt W=0.18u L=0.18u
12 Vin      G      0      PULSE(0      1.8 0 0 0 0.5n 1n 0)
13
14 * Analysis
15 .tran 0.1p 1n
16
17 * Results
18 .control
19 run
20 plot V(D) V(G)
21 .endc
```

22

23 .end

Results:

 


Figure 1: When $\frac{W}{L}$ ratios are as per Specifications and when there is no External-Load C_L .

Variation of t_p with Scaling Factor S :

As, the part of Scaling, Width of both N-MOSFET and P-MOSFET are increased by a factor of S .

S	t_{pHL} (in sec)	t_{pLH} (in sec)	$t_p = \frac{t_{pLH} + t_{pHL}}{2}$ (in sec)
1	1.84211×10^{-11}	0.7018×10^{-11}	1.271955×10^{-11}
2	2.1519×10^{-11}	0.63×10^{-11}	1.39095×10^{-11}
5	2.6744×10^{-11}	0.814×10^{-11}	1.7442×10^{-11}
7.5	2.75862×10^{-11}	0.8046×10^{-11}	1.78161×10^{-11}
10	2.7381×10^{-11}	0.8333×10^{-11}	1.7857×10^{-11}

When there is no External Load, the Propagation Delay (t_p) is almost negligible. So, there is no variation of t_p by changing Scaling Factor(S). When no External-Load is present Capacitance in Propagation Delay expression would be Drain Capacitance of both N-MOSFET and P-MOSFET whose values are very small. So, change in t_p will almost be negligible.

1.1.2 ii

SPICE Netlist:

```
1 Question-1a(ii)
2
3 * Model
4 .include "TSMC180.lib"
5 .model nch_tt nmos
6 .model pch_tt pmos
7
8 * Circuit
9 Vdd      S      0      DC      1.8
10 MP      D      G      S      S      pch_tt W=1.165u L=0.18u
11 MN      D      G      0      0      nch_tt W=0.18u L=0.18u
12 Vin     G      0      PULSE(0      1.8 0 0 0 0.5u 1u 0)
13 C       D      0      20p
14
15 * Analysis
16 .tran   1n      2u
17
18 * Results
19 .control
20 run
21 plot    V(D)    V(G)
22 .endc
23
24 .end
```

Results:

 


Figure 2: When $\frac{W}{L}$ ratios are as per Specifications and when there is External-Load $C_L = 20pF$.

Variation of t_p with Scaling Factor S :

As, the part of Scaling, Width of both N-MOSFET and P-MOSFET are increased by a factor of S .

S	t_{pHL} (in sec)	t_{pLH} (in sec)	$t_p = \frac{t_{pLH} + t_{pHL}}{2}$ (in sec)
1	1.07143×10^{-7}	0.64881×10^{-7}	0.86012×10^{-7}
2	0.692982×10^{-7}	0.34211×10^{-7}	0.517546×10^{-7}
4	0.408046×10^{-7}	0.17816×10^{-7}	0.293103×10^{-7}
6	0.280702×10^{-7}	0.12281×10^{-7}	0.201756×10^{-7}
8	0.219298×10^{-7}	0.0965×10^{-7}	0.157899×10^{-7}
10	0.184211×10^{-7}	0.07018×10^{-7}	0.1271955×10^{-7}

Plots:

 


Figure 3: t_p vs S

As Scaling increases, MOSFET Resistance decreases, which further decreases, t_p .

1.2 1b

Impact of W_p :

W_p effects t_{pLH} as Critical Path while charging of Load Capacitor happens through P-MOSFET.

Variation of t_p by scaling only P-MOSFET by a factor S :

S	t_{pHL} (in sec)	t_{pLH} (in sec)	t_p (in sec)
1	1.07143×10^{-7}	0.64881×10^{-7}	0.86012×10^{-7}
2	1.06322×10^{-7}	0.336392×10^{-7}	0.699806×10^{-7}
4	1.06322×10^{-7}	0.16667×10^{-7}	0.614945×10^{-7}
6	1.06322×10^{-7}	0.12069×10^{-7}	0.591955×10^{-7}
8	1.06322×10^{-7}	0.08621×10^{-7}	0.574715×10^{-7}
10	1.06322×10^{-7}	0.07471×10^{-7}	0.568965×10^{-7}

Results:

 


Figure 4: t_p vs S

Impact of W_n :

W_n effects t_{pHL} as Critical Path while discharging of Load Capacitor happens through N-MOSFET.

Variation of t_p by scaling only N-MOSFET by a factor S :

S	t_{pHL} (in sec)	t_{pLH} (in sec)	$t_p = \frac{t_{pLH} + t_{pHL}}{2}$ (in sec)
1	1.07143×10^{-7}	0.64881×10^{-7}	0.86012×10^{-7}
2	0.695402×10^{-7}	0.65517×10^{-7}	0.675286×10^{-7}
4	0.408046×10^{-7}	0.65517×10^{-7}	0.531608×10^{-7}
6	0.281609×10^{-7}	0.65517×10^{-7}	0.4683895×10^{-7}
8	0.218391×10^{-7}	0.65517×10^{-7}	0.4367805×10^{-7}
10	0.172414×10^{-7}	0.65517×10^{-7}	0.413792×10^{-7}

Results:

 


Figure 5: t_p vs S

2 Ring Oscillator

Specifications:

7-Stage Ring Oscillator by cascading Unit Inverters.

2.1 2a

SPICE Netlist:

```
1 Question-2
2
3 * Model
4 .include "TSMC180.lib"
5 .model nch_tt nmos
6 .model pch_tt pmos
7
8 * Circuit
9 Vdd      S      0      DC      1.8
10 MP1     D1     D7     S      S      pch_tt W=1.165u L=0.18u
11 MN1     D1     D7     0      0      nch_tt W=0.18u L=0.18u
12 C1      D1     0      20p
13 MP2     D2     D1     S      S      pch_tt W=1.165u L=0.18u
14 MN2     D2     D1     0      0      nch_tt W=0.18u L=0.18u
15 C2      D2     0      20p
16 MP3     D3     D2     S      S      pch_tt W=1.165u L=0.18u
17 MN3     D3     D2     0      0      nch_tt W=0.18u L=0.18u
18 C3      D3     0      20p
19 MP4     D4     D3     S      S      pch_tt W=1.165u L=0.18u
20 MN4     D4     D3     0      0      nch_tt W=0.18u L=0.18u
21 C4      D4     0      20p
22 MP5     D5     D4     S      S      pch_tt W=1.165u L=0.18u
23 MN5     D5     D4     0      0      nch_tt W=0.18u L=0.18u
24 C5      D5     0      20p
25 MP6     D6     D5     S      S      pch_tt W=1.165u L=0.18u
26 MN6     D6     D5     0      0      nch_tt W=0.18u L=0.18u
27 C6      D6     0      20p
28 MP7     D7     D6     S      S      pch_tt W=1.165u L=0.18u
29 MN7     D7     D6     0      0      nch_tt W=0.18u L=0.18u
30 C7      D7     0      20p
31
32
33 * Analysis
34 .tran 20p 20u
35
36 * Results
37 .control
38 run
39 plot V(D7)
40 .endc
41
42 .end
```

Time-Period and Frequency of Oscillations:


$$T = 1.8133 \times 10^{-6} \text{ sec}$$

(8)

$$f = 0.552080515 \text{ MHz}$$

(9)

Results:

 

2.2 2b

$$t_{pLH} = 0.16981 \times 10^{-6} \text{ s} \tag{10}$$

$$t_{pHL} = 0.16981 \times 10^{-6} \text{ s} \tag{11}$$

$$t_p = 0.16981 \times 10^{-6} \text{ s} \tag{12}$$

2.3 2c

By sizing up the the MOSFETs, Resistances of both P-MOS and N-MOS decrease which leads to decrease in Propagation Delay. This also increases Frequency of Oscillations.

2.4 2d

Instead of directly connecting the Output of Ring Oscillator to its Input, we can use a Switch to Start and Stop Oscillations.

When Switch is **ON**, there will be oscillations. When Switch is **OFF**, Output will remain in previous state.