

# Control Systems

G V V Sharma\*

## CONTENTS

1	Signal Flow Graph	1
2	Gain of Feedback Circuits	1
2.1	Estimation of Voltage Gain	1
3	Bode Plot	6
4	Second order System	6
5	Routh Hurwitz Criterion	6
6	State-Space Model	6
7	Nyquist Plot	6
8	Compensators	6
9	Gain Margin	6
10	Phase Margin	6
11	Oscillator	6
12	Root Locus	6
13	Polar Plot	6
14	PID Controller	6

**Abstract**—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/codes>

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

## 1 SIGNAL FLOW GRAPH

## 2 GAIN OF FEEDBACK CIRCUITS

2.1 Estimation of Voltage Gain  
2.1.1. Consider the Magnitude Bode Plot and Phase Bode Plot 2.1.1 of Open-Loop Transfer Function of an Amplifier. Estimate the Open-Loop Transfer Function. (Assume 'A' as 'G' and 'β' as 'H')

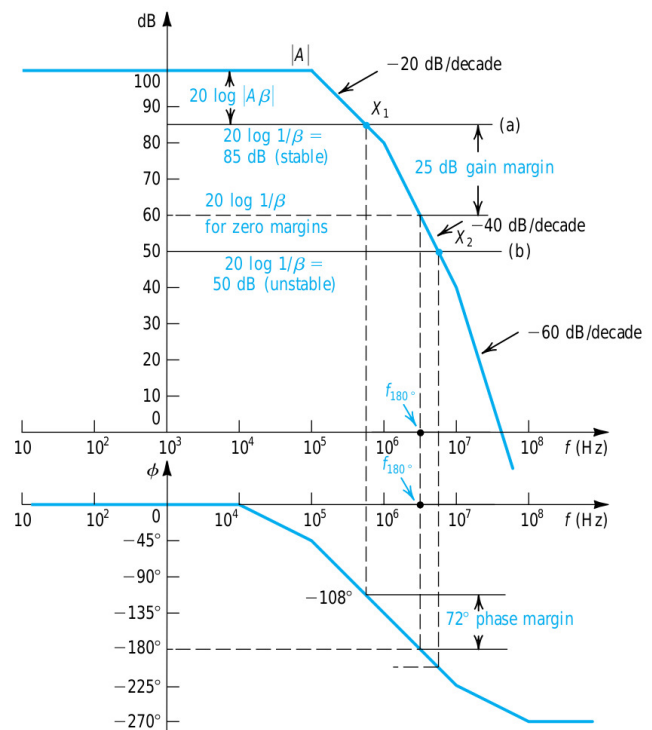


Fig. 2.1.1: Magnitude and Phase Bode Plot

**Solution:** Let  $G(f)$  be the Open-Loop Transfer Function,

$$G(f) = \begin{cases} 100 & 0 < f < 10^5 \\ 200 - 20\log(f) & 10^5 < f < 10^6 \\ 320 - 40\log(f) & 10^6 < f < 10^7 \\ 460 - 60\log(f) & 10^7 < f \end{cases} \quad (2.1.1.1)$$

$$\nabla G(f) = \frac{d(G(f))}{d(\log(f))} = \begin{cases} 0 & 0 < f < 10^5 \\ -20 & 10^5 < f < 10^6 \\ -40 & 10^6 < f < 10^7 \\ -60 & 10^7 < f \end{cases} \quad (2.1.1.2)$$

As we know that, **When a pole is encountered the slope always decreases by 20 dB/decade** and **When a zero is encountered the slope always increases by 20 dB/decade**. So, by observing 2.1.1 it can be concluded that we are having Poles at  $f = 10^5 \text{ Hz}$ ,  $10^6 \text{ Hz}$ ,  $10^7 \text{ Hz}$  and No Zeros.

So, the Open-Loop Transfer Function  $G(f)$  is

$$G(f) = \frac{10^5}{(1 + j\frac{f}{10^5})(1 + j\frac{f}{10^6})(1 + j\frac{f}{10^7})} \quad (2.1.1.3)$$

2.1.2. Calculate the Phase of Open-Loop Transfer Function.

**Solution:**

Phase of Open-Loop Transfer Function =  $\phi$

$$\phi = -\left[\tan^{-1}\left(f/10^5\right) + \tan^{-1}\left(f/10^6\right) + \tan^{-1}\left(f/10^7\right)\right] \quad (2.1.2.1)$$

2.1.3. Determine the Closed-Loop Voltage Gain of the System assuming  $|GH| \gg 1$  and also assuming the block diagram of Control System is 2.1.3

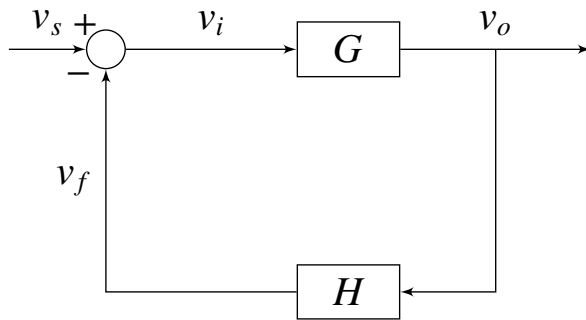


Fig. 2.1.3

**Solution:**

The Closed-Loop Voltage Gain of the Control System is

$$T = \frac{V_o}{V_s} = \frac{G}{1 + GH} \quad (2.1.3.1)$$

$$20 \log(T) = 20 \log(G) - 20 \log(1 + GH) \quad (2.1.3.2)$$

Considering the assumption  $|GH| \gg 1$ , It can be written as

$$20 \log(1 + GH) = 20 \log(GH) \quad (2.1.3.3)$$

So,

$$20 \log(T) = 20 \log(G) - 20 \log(GH) \quad (2.1.3.4)$$

$$20 \log(T) = -20 \log(H) \quad (2.1.3.5)$$

$$20 \log(T) = 20 \log\left(\frac{1}{H}\right) \quad (2.1.3.6)$$

$$T = \frac{1}{H} \quad (2.1.3.7)$$

So, The value of Closed-Loop Voltage Gain of the Control System under the assumption,  $|GH| \gg 1$  is  $T = \frac{1}{H}$

2.1.4. What is the value of Loop-Gain?

**Solution:**

The value of Loop-Gain can be calculated by the difference of 2-curves  $20 \log |A|$  and  $20 \log(\frac{1}{H})$ . The difference between the two curves will be

$$20 \log |G| - 20 \log \frac{1}{H} = 20 \log |GH| \quad (2.1.4.1)$$

2.1.5. Define Phase-Margin

**Solution:**

**Phase-Margin:** The phase margin is defined as the angle in degrees by which the phase angle is smaller than  $-180^\circ$  at the gain crossover, the gain crossover being the frequency at which the open-loop gain first reaches 1.

2.1.6. Find the frequencies for which phase margins are  $90^\circ$  and  $45^\circ$  respectively?

**Solution:**

Let Phase Margin be  $\alpha = 90^\circ$ . Then,

$$\alpha = \phi - (-180^\circ) \quad (2.1.6.1)$$

$$\phi = -180^\circ + \alpha \quad (2.1.6.2)$$

$$\phi = -90^\circ \quad (2.1.6.3)$$

So, by the definition of Phase-Margin, at  $\phi = -90^\circ$ ,  $|GH| = 1$ . The value of  $\phi = -90^\circ$  between poles  $f = 10^5 \text{ Hz}$ ,  $10^6 \text{ Hz}$ . Assuming the Poles are farther apart,

$$\tan^{-1}\left(\frac{f}{10^7}\right) \approx 0 \quad (2.1.6.4)$$

where  $10^5 < f < 10^6$

So,

$$-\tan^{-1}(f/10^5) - \tan^{-1}(f/10^6) = -90 \quad (2.1.6.5)$$

$$\tan^{-1}(f/10^5) + \tan^{-1}(f/10^6) = 90 \quad (2.1.6.6)$$

$$\tan^{-1}(f/10^5) = 90 - \tan^{-1}(f/10^6) \quad (2.1.6.7)$$

$$\tan^{-1}(f/10^5) = \cot^{-1}(f/10^6) \quad (2.1.6.8)$$

$$\tan^{-1}(f/10^5) = \tan^{-1}(10^6/f) \quad (2.1.6.9)$$

$$f^2 = 10^{11} \quad (2.1.6.10)$$

$$f = 3.162 \times 10^5 \quad (2.1.6.11)$$

So, the approximate value of  $f$  at which Phase Margin is  $90^\circ$  is  $f = 3.162 \times 10^5 \text{ Hz}$ .

Similarly let Phase Margin be  $\alpha = 45^\circ$ . Then,

$$\alpha = \phi - (-180^\circ) \quad (2.1.6.12)$$

$$\phi = -180^\circ + \alpha \quad (2.1.6.13)$$

$$\phi = -135^\circ \quad (2.1.6.14)$$

So, by the definition of Phase-Margin, at  $\phi = -135^\circ$ ,  $|GH| = 1$ . The value of  $\phi = -135^\circ$  approximately at poles  $f = 10^6 \text{ Hz}$ .

So, the approximate value of  $f$  at which Phase Margin is  $45^\circ$  is  $f = 10^6$ .

2.1.7. Find the minimum values of Closed-Loop Voltage Gain for which phase margins are  $90^\circ$  and  $45^\circ$  respectively

**Solution:**

For  $\alpha = 90^\circ$ ,

$$f = 3.162 \times 10^5 \quad (2.1.7.1)$$

By substituting  $f$  in Open-Loop Gain  $G(f)$

(assuming poles are far part),

$$G(f) = 200 - 20\log(3.162 \times 10^5) \quad (2.1.7.2)$$

$$G(f) = 90 \text{ dB} \quad (2.1.7.3)$$

$$G = 3.1625 \times 10^4 \quad (2.1.7.4)$$

At that  $f = 3.162 \times 10^5$ ,

$$H = \frac{1}{G} \quad (2.1.7.5)$$

$$H = 3.162 \times 10^{-5} \quad (2.1.7.6)$$

The minimum value of Closed-Loop Gain occurs at  $|GH| \gg 1$  and the value of Closed-Loop Gain is  $T = \frac{1}{H}$

$$T = \frac{1}{H} = 3.1625 \times 10^4 \quad (2.1.7.7)$$

**So, The minimum value of Closed-Loop Gain with Phase Margin equal to  $\alpha = 90^\circ$  is  $T_{min} = 3.1625 \times 10^4$ .**

For  $\alpha = 45^\circ$ ,

$$f = 10^6 \quad (2.1.7.8)$$

By substituting  $f$  in Open-Loop Gain  $G(f)$  (assuming poles are far part),

$$G(f) = 200 - 20\log(10^6) \quad (2.1.7.9)$$

$$G(f) = 80 \text{ dB} \quad (2.1.7.10)$$

$$G = 10^4 \quad (2.1.7.11)$$

At that  $f = 10^6$ ,

$$H = \frac{1}{G} \quad (2.1.7.12)$$

$$H = 10^{-4} \quad (2.1.7.13)$$

The minimum value of Closed-Loop Gain occurs at  $|GH| \gg 1$  and the value of Closed-Loop Gain is  $T = \frac{1}{H}$

$$T = \frac{1}{H} = 10^4 \quad (2.1.7.14)$$

**So, The minimum value of Closed-Loop Gain with Phase Margin equal to  $\alpha = 45^\circ$  is  $T_{min} = 10^4$ .**

2.1.8. Break the Transfer Function  $G(f)$  into Simple Blocks and Create a Block Diagram for  $G(f)$ .

**Solution:**

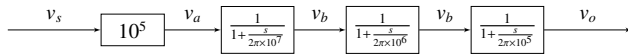


Fig. 2.1.8

2.1.9. Find the Gain of RC-Circuit shown below 2.1.9 and also identify the location of Poles.

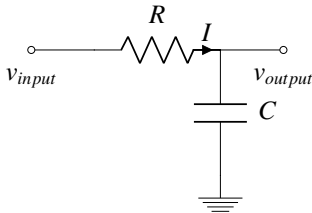


Fig. 2.1.9

**Solution:**

$$I = \frac{v_{input}}{R + \frac{1}{Cs}} \quad (2.1.9.1)$$

$$v_{output} = I \times \frac{1}{Cs} \quad (2.1.9.2)$$

$$v_{output} = \frac{v_{input} \times \frac{1}{Cs}}{R + \frac{1}{Cs}} \quad (2.1.9.3)$$

$$\frac{v_{output}}{v_{input}} = \frac{1}{RCs + 1} \quad (2.1.9.4)$$

$$s = j2\pi f \quad (2.1.9.5)$$

$$\text{Gain} = \frac{v_{output}}{v_{input}} = \frac{1}{j2\pi RCf + 1} \quad (2.1.9.6)$$

So, there is a Pole at frequency  $f = \frac{1}{2\pi RC}$  for the Transfer Function of Gain.

2.1.10. Find the Gain of Small-Signal of Operational Amplifier. The circuit diagram of Small-Signal Model is 2.1.10.

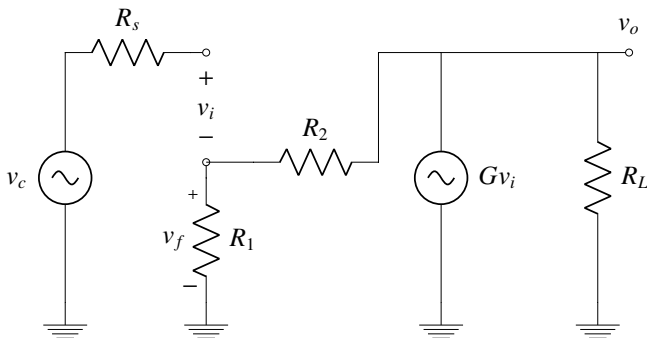


Fig. 2.1.10

**Solution:**

Applying KVL and KCL,

$$v_o = Gv_i \quad (2.1.10.1)$$

As no current flows through  $R_s$ ,

$$v_i = v_c - v_f \quad (2.1.10.2)$$

$$v_f = \frac{R_1}{R_1 + R_2} v_o \quad (2.1.10.3)$$

$$v_i = \frac{v_o}{G} \quad (2.1.10.4)$$

$$\frac{v_o}{G} = v_c - \frac{R_1}{R_1 + R_2} v_o \quad (2.1.10.5)$$

$$\frac{v_o}{v_c} = \frac{G}{1 + G \frac{R_1}{R_1 + R_2}} \quad (2.1.10.6)$$

So, Gain of the Circuit is  $\frac{G}{1 + G \frac{R_1}{R_1 + R_2}}$

2.1.11. Design a Circuit Model that follows the Transfer Function  $G(f)$

**Solution:**

Our Design for Modelling the Transfer Function is based on Poles of RC-Circuit and Gain of Operational Amplifier.

So, the Circuit Diagram is,

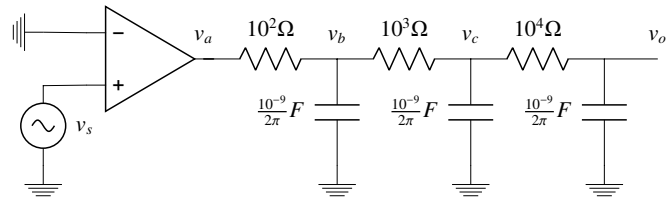


Fig. 2.1.11

Assuming, Gain of Operational Amplifier is  $10^5$ .

Small Signal Model of the circuit is

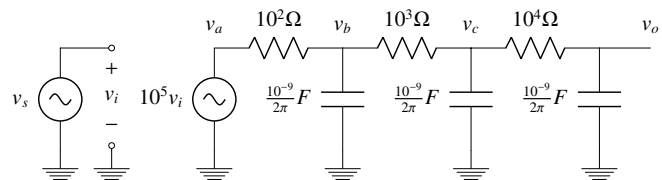


Fig. 2.1.11

The cascade of RC Circuits are used to introduce poles in the circuit and Op-Amp are used to achieve the Gain required.

At the Operational Amplifier,

$$v_i = v_s \quad (2.1.11.1)$$

$$v_a = 10^5 v_i \quad (2.1.11.2)$$

$$v_a = 10^5 v_s \quad (2.1.11.3)$$

At the first RC-Circuit,

$$2\pi RC = 10^{-7} \quad (2.1.11.4)$$

$$v_b = \frac{v_a}{1 + j\frac{f}{10^7}} \quad (2.1.11.5)$$

$$v_b = \frac{10^5 v_i}{1 + j\frac{f}{10^7}} \quad (2.1.11.6)$$

At the second RC-Circuit,

$$2\pi RC = 10^{-6} \quad (2.1.11.7)$$

$$v_c = \frac{v_b}{1 + j\frac{f}{10^6}} \quad (2.1.11.8)$$

$$v_c = \frac{10^5 v_i}{(1 + j\frac{f}{10^6})(1 + j\frac{f}{10^7})} \quad (2.1.11.9)$$

At the third RC-Circuit,

$$2\pi RC = 10^{-5} \quad (2.1.11.10)$$

$$v_o = \frac{v_c}{1 + j\frac{f}{10^5}} \quad (2.1.11.11)$$

$$v_o = \frac{10^5 v_i}{(1 + j\frac{f}{10^5})(1 + j\frac{f}{10^6})(1 + j\frac{f}{10^7})} \quad (2.1.11.12)$$

The RC Circuits introduces poles at  $f = 10^7 \text{ Hz}$ ,  $10^6 \text{ Hz}$ ,  $10^5 \text{ Hz}$  respectively from left to right and Op-Amp introduced a Gain =  $10^5$ . So, the value of  $v_o$  is

$$v_o = \frac{10^5 v_i}{(1 + j\frac{f}{10^5})(1 + j\frac{f}{10^6})(1 + j\frac{f}{10^7})} \quad (2.1.11.13)$$

So, Open-Loop Gain is

$$G = \frac{10^5}{(1 + j\frac{f}{10^5})(1 + j\frac{f}{10^6})(1 + j\frac{f}{10^7})} \quad (2.1.11.14)$$

2.1.12. Design a Circuit Model that follows the Feedback Transfer Function  $H(f)$

**Solution:**

On Bode Plot is  $H$  is independent of frequency. So,  $H$  should not involve any Reactive Elements. So,  $H$  is a combination of Resistors or a Voltage Divider.

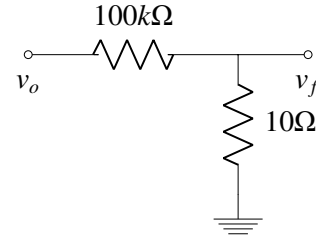


Fig. 2.1.12

$$v_f = \frac{10}{10 + 10^5} \times v_o \quad (2.1.12.1)$$

$$v_f \approx 10^{-4} v_o \quad (2.1.12.2)$$

$$\frac{v_f}{v_o} \approx 10^{-4} \quad (2.1.12.3)$$

$$H(f) = 10^{-4} \quad (2.1.12.4)$$

2.1.13. Design a Closed-Loop Transfer Function by combining both the Open-Loop and Feedback Circuits. Also draw its Small-Signal Model

**Solution:**

The Closed-Loop Circuit is

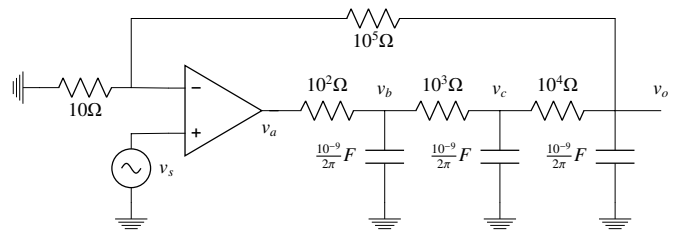


Fig. 2.1.13

The Small-Signal Model of Closed-Loop Circuit is

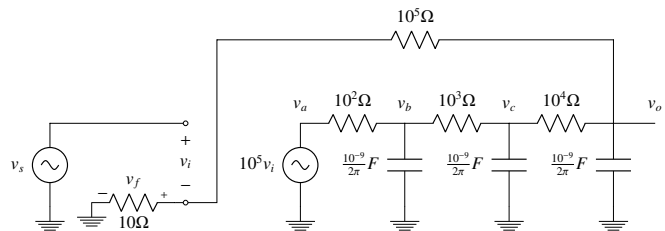


Fig. 2.1.13

From the Small-Signal Model 2.1.13,

$$G = \frac{v_o}{v_i} = \frac{10^5}{\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{10^6}\right)\left(1 + j\frac{f}{10^7}\right)} \quad (2.1.13.1)$$

$$H = \frac{v_f}{v_o} = 10^{-4} \quad (2.1.13.2)$$

The Closed-Loop Gain,

$$v_i = v_s - v_f \quad (2.1.13.3)$$

$$\frac{v_o}{G} = v_s - Hv_o \quad (2.1.13.4)$$

$$\frac{v_o}{v_s} = \frac{G}{1 + GH} \quad (2.1.13.5)$$

So, the Closed-Loop Gain,

$$T = \frac{v_o}{v_s} = \frac{10^5}{10 + \left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{10^6}\right)\left(1 + j\frac{f}{10^7}\right)} \quad (2.1.13.6)$$

### 3 BODE PLOT

### 4 SECOND ORDER SYSTEM

### 5 ROUTH HURWITZ CRITERION

### 6 STATE-SPACE MODEL

### 7 NYQUIST PLOT

### 8 COMPENSATORS

### 9 GAIN MARGIN

### 10 PHASE MARGIN

### 11 OSCILLATOR

### 12 ROOT LOCUS

### 13 POLAR PLOT

### 14 PID CONTROLLER