

EE2015: ASSIGNMENT 2 - SYNTHESIS OF FILTERS

Deadline: Fri, 4th Oct, 10:00 PM

1. Synthesis of Analog Filters

In this experiment you will characterize an analog filter provided to you. Perform the following tasks and submit your results/report on Acadly.

- (a) Plot the frequency response of the circuit on a graph sheet, and calculate the pass and stop band frequencies (pass band gain ≥ -3 dB and stop band gain ≤ -10 dB. What are the factors that impact the limits of measurable gain in your experiment, if any?
- (b) Obtain the transfer function of the filter based on its frequency response using (a) Butterworth filter design and (b) Chebyshev type I filter design.
- (c) Synthesize the obtained transfer functions using RC circuits.
- (d) Choose a square wave input signal of appropriate frequency and observe the variation of output as a function of frequency. Explain the observed behavior.
- (e) Choose a square wave of appropriate frequency and determine the frequency spectrum of (a) input and (b) output (when the frequency of square wave is in pass and stop bands).
- (f) *Thought experiment:* A filter will have both amplitude and phase response. How would you characterize the phase response in the lab?